

**Amirkabir University of Technology**  
**(Tehran Polytechnic)**


# **Electronics3**

Dr. Yavari

Mohammad Javad Ranjbar9523048

Summer99

Information:

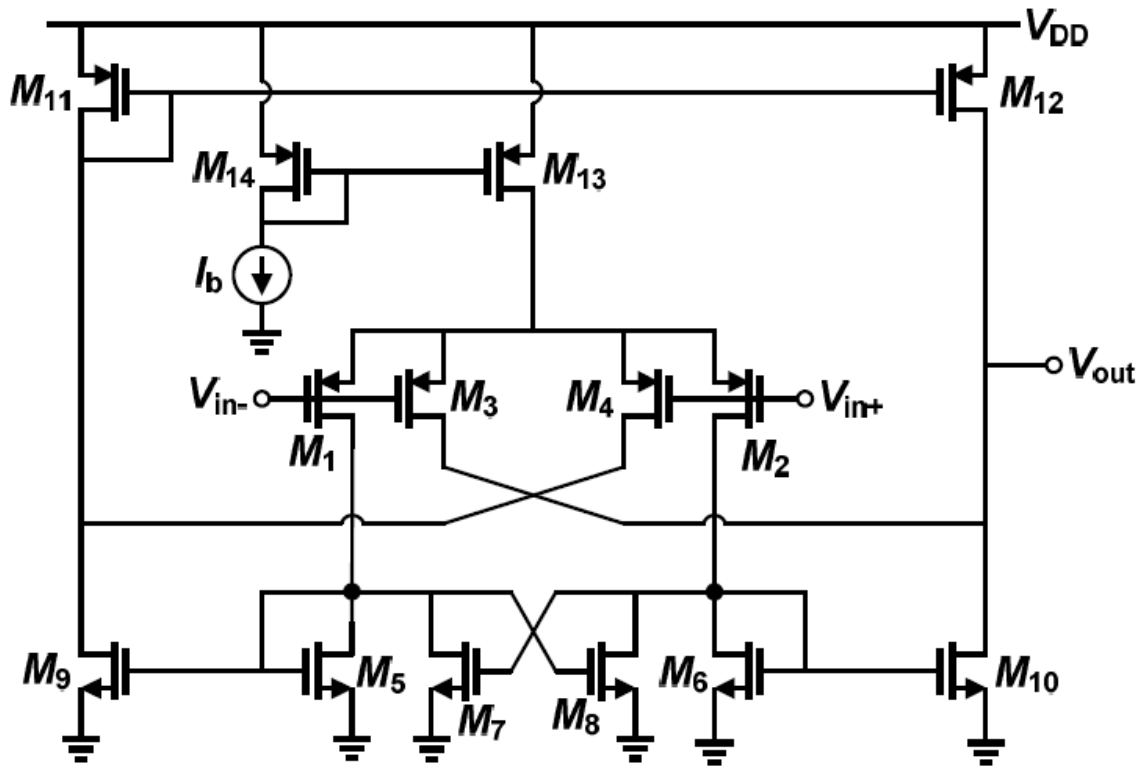

- Open-loop DC gain  $\geq 25$  V/V
- Output voltage swing  $\geq 0.5$  V<sub>pp</sub>
- CMRR  $\geq 35$  dB
- Settling time with 0.2% settling error in unity-gain sample & hold configuration  $\leq 4$  ns
- Load capacitance:  $C_L = 1$  pF
- Sample & hold capacitance:  $C_H = 1$  pF
- Input common-mode voltage:  $V_{cmi} = 0.3$  V
- Output common-mode voltage:  $V_{cmo} = 0.5$  V
- Ideal DC voltage:  $V_{dc} = 0.2$  V
- Power supply voltage:  $V_{DD} = 1.0$  V
- Power dissipation: as low as possible
- Technology: 90 nm CMOS

## Design:

We designed the circuit using the above information and entered the numbers obtained in the software ,but the results were not obtained according to the design and a number of transistors were in the linear and cut-off area and the amount of gain and phase margin was less ,so we must We changed the design a bit to achieve the desired result ,so with experimental changes we tried the execution and made changes to get new results.

## Initial design:

M1	1	Vin-	3	dd	pch	w=1.02u	l=100n	m=29
M2	4	Vin+	3	dd	pch	w=1.02u	l=100n	m=29
M3	Vout	Vin-	3	dd	pch	w=1.02u	l=100n	m=29
M4	2	Vin+	3	dd	pch	w=1.02u	l=100n	m=29
M5	1	1	ss	ss	nch	w=1.05u	l=100n	m=5
M6	4	4	ss	ss	nch	w=1.05u	l=100n	m=5
M7	1	4	ss	ss	nch	w=1.481u	l=100n	m=10
M8	4	1	ss	ss	nch	w=1.481u	l=100n	m=10
M9	2	1	ss	ss	nch	w=1.02u	l=100n	m=29
M10	Vout	4	ss	ss	nch	w=1.02u	l=100n	m=29
M11	2	2	dd	dd	pch	w=0.888u	l=100n	m=100
M12	Vout	2	dd	dd	pch	w=0.888u	l=100n	m=100
M13	3	Vb	dd	dd	pch	w=0.52u	l=100n	m=100
M14	Vb	Vb	dd	dd	pch	w=1.18u	l=100n	m=10

## Preliminary design results:

subckt

element 0:m13 0:m14

model 0:pch.15 0:pch.10

region Saturati Saturati

id -675.8475u -199.9964u

ibs 0. 0.

ibd 27.4244p 4.4002p

vgs -440.0156m -440.0156m

vds -274.2425m -440.0156m

gain= 1.9605E+01

unity\_gain= 5.2808E+09

phase\_margin= 5.1642E+00

subckt

element 0:m7 0:m8 0:m9 0:m10 0:m11 0:m12

model 0:nch.8 0:nch.8 0:nch.8 0:nch.8 0:pch.15 0:pch.15

region Cutoff Cutoff Cutoff Cutoff Saturati Saturati

id 166.3552u 166.3552u 498.2067u 498.2047u -381.2198u -381.2214u

ibs 0. 0. 0. 0. 0. 0.

ibd -3.4396p -3.4396p -18.6769p -18.6769p 35.5980p 35.5984p

vgs 343.9433m 343.9433m 343.9433m 343.9433m -355.9773m -355.9773m

vds 343.9433m 343.9433m 644.0227m 644.0196m -355.9773m -355.9804m

subckt

element 0:m1 0:m2 0:m3 0:m4 0:m5 0:m6

model 0:pch.10 0:pch.10 0:pch.10 0:pch.10 0:nch.8 0:nch.8

region Saturati Saturati Saturati Saturati Cutoff Cutoff

id -220.9372u -220.9372u -116.9848u -116.9824u 54.5809u 54.5809u

ibs 7.9531p 7.9531p 7.9531p 7.9531p 0. 0.

ibd 19.0258p 19.0258p 10.3235p 10.3234p -1.7198p -1.7198p

vgs -425.7575m -425.7575m -425.7575m -425.7575m 343.9433m 343.9433m

vds -381.8143m -381.8143m -81.7379m -81.7348m 343.9433m 343.9433m

Design after changes:

M1	1	Vin-	3	dd	pch	w=1.02u	l=100n	m=29
M2	4	Vin+	3	dd	pch	w=1.02u	l=100n	m=29
M3	Vout	Vin-	3	dd	pch	w=1.02u	l=100n	m=29
M4	2	Vin+	3	dd	pch	w=1.02u	l=100n	m=29
M5	1	1	ss	ss	nch	w=1.05u	l=100n	m=4
M6	4	4	ss	ss	nch	w=1.05u	l=100n	m=4
M7	1	4	ss	ss	nch	w=1.481u	l=100n	m=3
M8	4	1	ss	ss	nch	w=1.481u	l=100n	m=3
M9	2	1	ss	ss	nch	w=1.02u	l=100n	m=120
M10	Vout	4	ss	ss	nch	w=1.02u	l=100n	m=120
M11	2	2	dd	dd	pch	w=0.888u	l=100n	m=40
M12	Vout	2	dd	dd	pch	w=0.888u	l=100n	m=40
M13	3	Vb	dd	dd	pch	w=0.52u	l=100n	m=100
M14	Vb	Vb	dd	dd	pch	w=1.18u	l=100n	m=10
Ib	Vb	dd	dc=200u					
VDD	dd	0	dc=1					
VSS	ss	0	dc=0					

Results after changes:

gain= 3.1033E+01  
unity\_gain= 5.1556E+09  
phase\_margin= 6.7645E+01

subckt

element 0:m13 0:m14  
model 0:pch.15 0:pch.10  
region Saturati Saturati  
id -683.5266u -199.9965u  
ibs 0. 0.  
ibd 28.4371p 4.4002p  
vgs -440.0156m -440.0156m  
vds -284.3695m -440.0156m

subckt

element 0:m7 0:m8 0:m9 0:m10 0:m11 0:m12  
model 0:nch.8 0:nch.8 0:nch.8 0:nch.8 0:pch.15 0:pch.15  
region Saturati Saturati Saturati Saturati Saturati Saturati  
id 92.0080u 92.0080u 2.4338m 2.4338m -2.2654m -2.2654m  
ibs 0. 0. 0. 0. 0. 0.  
ibd -1.1343p -1.1343p -47.6996p -47.6994p 24.1007p 24.1007p  
vgs 378.0890m 378.0890m 378.0890m 378.0890m -602.5133m -602.5133m  
vds 378.0890m 378.0890m 397.4867m 397.4852m -602.5133m -602.5148m

```

subckt
element 0:m1  0:m2  0:m3  0:m4  0:m5  0:m6
model  0:pch.10 0:pch.10 0:pch.10 0:pch.10 0:nch.8 0:nch.8
region Saturati Saturati Saturati Saturati Saturati Saturati
id  -173.3389u -173.3389u -168.4217u -168.4214u 81.3256u 81.3256u
ibs  8.2468p 8.2468p 8.2468p 8.2468p 0. 0.
ibd  18.0355p 18.0355p 17.4730p 17.4730p -1.5124p -1.5124p
vgs  -415.6305m -415.6305m -415.6305m -415.6305m 378.0890m 378.0890m
vds  -337.5415m -337.5415m -318.1453m -318.1439m 378.0890m 378.0890m

```

```

subckt
element 0:m1  0:m2  0:m3  0:m4  0:m5  0:m6
model  0:pch.10 0:pch.10 0:pch.10 0:pch.10 0:nch.8 0:nch.8
region Saturati Saturati Saturati Saturati Saturati Saturati
id  -173.3389u -173.3389u -168.4217u -168.4214u 81.3256u 81.3256u
ibs  8.2468p 8.2468p 8.2468p 8.2468p 0. 0.
ibd  18.0355p 18.0355p 17.4730p 17.4730p -1.5124p -1.5124p
vgs  -415.6305m -415.6305m -415.6305m -415.6305m 378.0890m 378.0890m
vds  -337.5415m -337.5415m -318.1453m -318.1439m 378.0890m 378.0890m

```

So the circuit has obtained the desired values

For swinging ,we apply a sinusoidal input to the circuit so that the output wave does not break





Transient mode response:


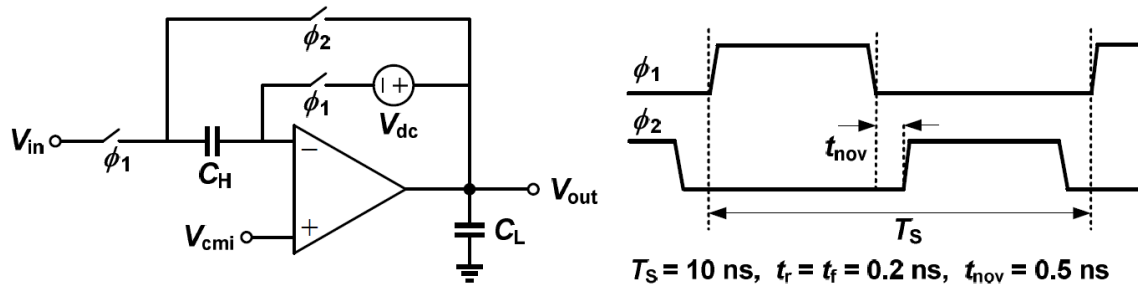



Fig. 2: Transient simulation circuit.

We need to add two capacitors and a switch that have two phase difference switches and follow the input output with phase difference.

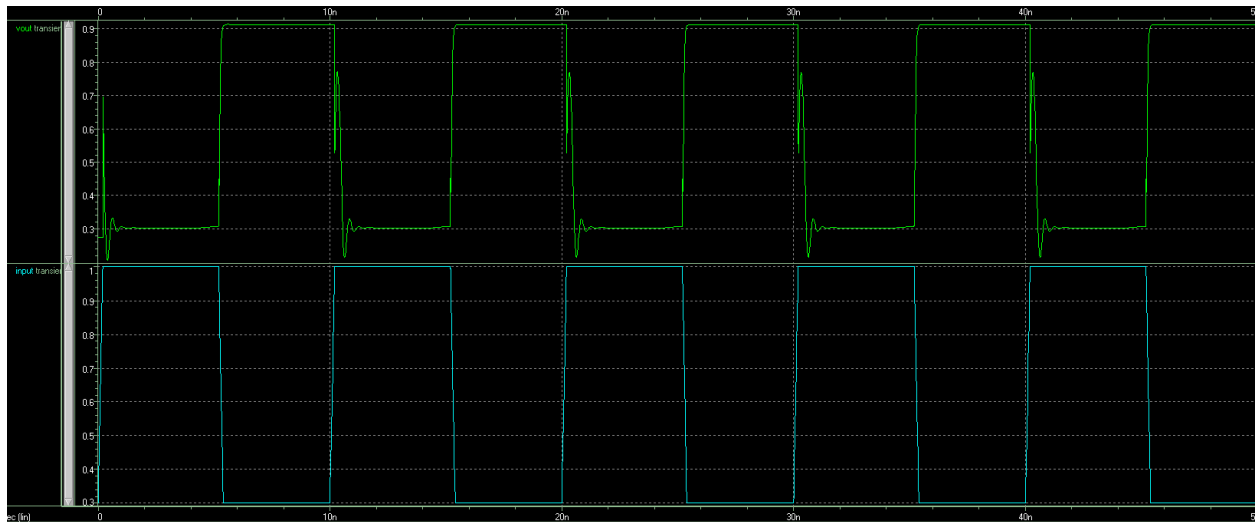The settling time is about one nanosecond



Theoretical calculations:

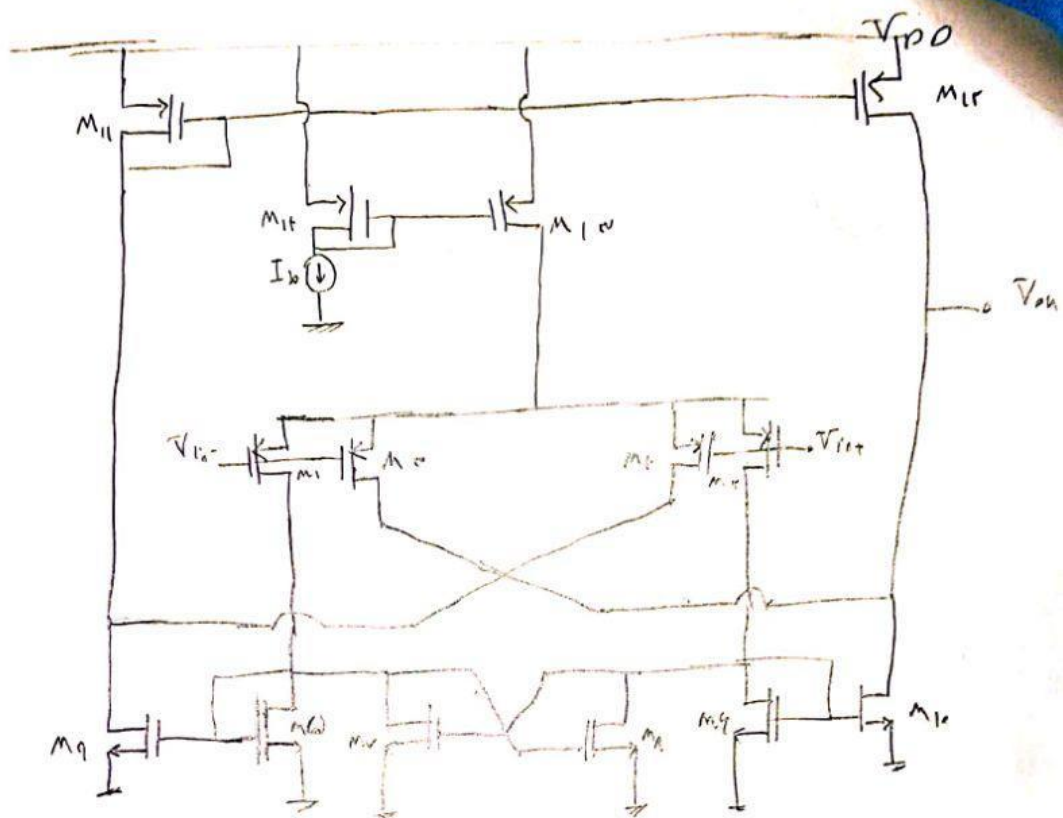

$$\left(\frac{W}{L}\right)_{1r} = 10 \left(\frac{W}{L}\right)_{1f} \quad \left(\frac{W}{L}\right)_{12} = 1 \left(\frac{W}{L}\right)_{13} \quad \left(\frac{W}{L}\right)_{14} = 10 \left(\frac{W}{L}\right)_{15}$$

$$\left(\frac{W}{L}\right)_{11} = \left(\frac{W}{L}\right)_{1r} \Rightarrow I_{D11} = \frac{\left(\frac{W}{L}\right)_{12}}{\left(\frac{W}{L}\right)_{1r}} \times I_{ref} = 1 \text{ mA}$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = 0.1 \text{ mA} \quad g_{m(1,2,3,4)} = \frac{2 I_{D1}}{V_{eff}} = 4.4 \text{ mS}$$

$$I_{D5} = I_{D6} = 0.1 \text{ mA} \Rightarrow I_{D7} = I_{D8} = 0.1 \text{ mA} \quad g_{m(5,6)} = 2 \times 1.1 \text{ mS}$$

$$I_{D9} = I_{D10} = \frac{\left(\frac{W}{L}\right)_9}{\left(\frac{W}{L}\right)_5} \times I_{D5} = 1 \text{ mA} \quad g_{m(9,10)} = 1.1 \text{ mS} \quad g_{m(11,12)} = 2.2 \text{ mS}$$

$$I_{D11} = I_{D12} = -I_{D7} + I_{D9} = 1.1 \text{ mA} \quad g_{m(11,12)} = 2.2 \text{ mS}$$

$$g_{m(13)} = 2.2 \text{ mS} \quad g_{m(14)} = 2.2 \text{ mS} \quad r_{ds13} = 2 \text{ K}\Omega \quad r_{ds14} = 2 \text{ K}\Omega$$

$$r_{ds}(1,1,r) = \frac{1}{\lambda I_{D1}} = 2.1 K \Omega$$

$$r_{ds}(2,1) = 2 K \Omega$$

$$r_{ds}(1,1) = 100 K \Omega$$

$$r_{ds}(1,1) = 2 K \Omega$$

$$r_{ds}(11,1) = 4.44 K \Omega$$

$$R_{out} = r_{ds1r} \parallel r_{ds2r} \parallel r_{ds11} = 2.1 K \Omega \parallel 2 K \Omega \parallel 4.44 K \Omega = 1.2 K \Omega$$

$$I_{sc} = i_{d1r} + i_{d11} - i_{d1r}$$

$$i_{d1r} = (0 + \frac{V_{in}}{r}) g_{m1} = 1.1 \mu m V_{in}$$

$$i_{d1r} = i_{d1} + i_{d11} \Rightarrow (1 - \frac{V_{in}}{r}) g_{m1} = V_A g_{c1} - V_A g_{m1}$$

$$-1.1 \mu m V_{in} = V_A (2.1 \mu m - 1.1 \mu m)$$

$$V_A = - \frac{1.1 \mu m V_{in}}{f} = -0.11 \mu m V_{in}$$

$$i_{d11} = V_A g_{m11} = -1.1 \mu m V_{in}$$

$$i_{d1} = -V_A g_{m1} = 1.1 \mu m V_{in}$$

$$i_{d11} = i_{d1} - i_{d1r}$$

$$i_{d1r} = i_{d1} = 1.1 \mu m (V_{in}) + 1.1 \mu m V_{in} = 2.2 \mu m (V_{in})$$

$$i_{d1r} = i_{d11} = 2.2 \mu m V_{in}$$

$$I_{sc} = (1.1 \mu m - 1.1 \mu m - 2.2 \mu m) V_{in} = -1.1 \mu m = G_m$$

$$A_{de} = -G_m R_{out} = 1.1 \mu m \times 1.2 K = 11.0 \mu$$

$$I_{sc}' = i_{d1}' + i_{dr}' - i_{di}'$$

$$\frac{v_n - v_n}{r_{di'r}} = f(v_n - v_{cm}) g_{m1} \Rightarrow v_n = 0,99 v_{cm}$$

$$i_{dr} = i_{di} = (v_n - v_{cm}) g_{m1} = 9,44 \times 10^{-6} v_{in}$$

$$i_{di} = i_{da} + i_{dv} = 9,44 \times 10^{-6} v_{in} = -v_B (\omega_1 r_{r1} + 1 r_{r2}) \times 10^{-5}$$

$$v_B = 0,01 v_{in}$$

$$i_{dq} = v_B g_{m1} = 9,44 \times 10^{-6} v_{in}$$

$$i_{di1} = i_{dq} - i_{dt} = 9,44 \times 10^{-6} v_{in} = i_{di'r}$$

$$i_{di1} = v_B g_{m10} = 9,44 \times 10^{-6} v_{in}$$

$$I_{sc} = (9,44 + 9,44 - 9,44) \times 10^{-6} v_{in} = 17,77 \times 10^{-6} v_{in}$$

$$G_m = 17,77 \times 10^{-6}$$

$$A_{cm} = -G_m R_{out} = 0,1777 \text{ V/V}$$

$$CMMR = 20 \log \frac{A_{dm}}{A_{cm}} = 20 \log \frac{11,90}{0,1777} = 20,7 > 20$$

$$\omega_{p1} = \frac{1}{C_L R_{out}} = \frac{1}{10 \times 10^{-6} \times 10^3} = 1 \times 10^4 \text{ rad/s}$$

$$\omega_t = \omega_{p1, A_{de}} = 1 \times 10^4 \times 11,90 = 1,19 \times 10^5 \text{ rad/s}$$

$$SR^+ \Rightarrow M_1, M_2: \text{off} \Rightarrow M_4, M_5: \text{off} \Rightarrow M_{11}: \text{off}, M_{12}, M_{13}: \text{on}$$

$$I_{D1}^{r_{MA}} = I_{D1} + I_{D2} = 2 I_{D1} \Rightarrow I_{D1} = 1 \text{ mA} \Rightarrow I_{D1} = I_{D2}$$

(2)



$$I_{D1} = I_{D1}^{f_{ov}} + I_{D1} = 1 \text{ mA} \Rightarrow I_{D1} = 0,1 \text{ mA} \Rightarrow I_{D1} = 0,1 \text{ mA}$$

$$I_{D1} = \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2} \times I_{D2} = 1 \text{ mA}$$

$$I_{D11} = I_{D1} - I_{D1}^2 = 1 \text{ mA} \Rightarrow I_{D11} = I_{D12} = 1 \text{ mA}$$

$$I_{C1} = I_{D1} - I_{D1} = 1 - 1 = 0 \text{ mA}$$

$$(SR)^+ = \frac{I_{C1}}{C_1} = \frac{\omega_m}{1P} = \omega \times 1,9 \frac{V}{S}$$

$$(SR)^- \Rightarrow M(1, 1, 0, 1, 1) : off \quad M_1, M_2 : on$$

$$I_{D1} = I_{D1} = 1 \text{ mA} \quad I_{D1} = I_{D1} + I_{D1} \Rightarrow I_{D1} = 0,1 \text{ mA}$$

$$I_{D1} = 0,1 \text{ mA} \quad I_{D1} = 0,1 \text{ mA} = 1 \text{ mA}$$

$$I_{D11} = -I_{D1} = -1 \text{ mA} \quad I_{D11} = I_{D1} = -1 \text{ mA}$$

$$I_{C1} = 1 \text{ mA} + 1 \text{ mA} = 2 \text{ mA}$$

$$(SR)^- = \frac{\omega_m}{1P} = \omega \times 1,9 \frac{V}{S}$$

$$t_s = \frac{\Delta V - \sqrt{V_{ref}}}{SR} - \frac{1}{B_{u4}} \ln\left(\frac{\delta V}{1}\right)$$

$$= \frac{1 - \sqrt{V_{ref}}}{\omega \times 1,9} - \frac{1}{B_{u4} \times 1,9} \ln(V_{ref}) \Rightarrow$$

$$0,10 \text{ ns} + 1,1 \text{ ns} = 1,2 \text{ ns}$$

(F)

$$\mu_{nCox} = 4 \cdot \frac{\mu A}{V}, \quad \mu_{pCox} = 120, \quad L_{min} = 0.1 \mu m$$

$$\left(\frac{W}{L}\right) = \frac{I_{Dp}}{\mu_{nCox} V_{eff}}, \quad \left(\frac{W}{L}\right)_{1f} = \frac{I_{D1}}{10 \times (1.1)^2} = 11.11$$

$$W_{1f} = 11.11 \mu m, \quad \left(\frac{W}{L}\right)_{1r} = \frac{I_{D1}}{10 \times 0.25} = 22.22 \Rightarrow W_{1r} = 22.22 \mu m$$

$$\left(\frac{W}{L}\right)_{1,r,cf} = \frac{1000}{10 \times 0.25} = 299.29 \Rightarrow W_{1,r,cf} = 29.429 \mu m$$

$$\left(\frac{W}{L}\right)_{2,4} = \frac{100}{40 \times 0.25} = 25.9 \Rightarrow W_{2,4} = 2.59 \mu m$$

$$\left(\frac{W}{L}\right)_{v,1} = \frac{I_{D1}}{40 \times 0.25} = 11.11, \quad W_{v,1} = 1.11 \mu m$$

$$\left(\frac{W}{L}\right)_{h,1} = \frac{I_{D1}}{40 \times 0.25} = 299.29 \Rightarrow W_{h,1} = 29.429 \mu m$$

$$\left(\frac{W}{L}\right)_{11,1} = \frac{I_{D1}}{90 \times 0.25} = 111.11 \Rightarrow W_{11,1} = 11.11 \mu m$$